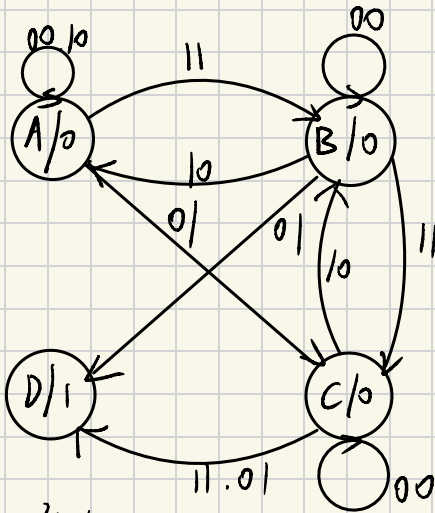


# 大作业(2)

## ①原始状态图



## 原始状态表

现态	次态				输出
	$X_1=0, X_2=0$	$X_1=0, X_2=1$	$X_1=1, X_2=1$	$X_1=1, X_2=0$	
A	A	C	B	A	0
B	B	D	C	A	0
C	C	D	D	B	0
D	D	D	D	D	1

BC  
AB  
BCD

编码:

	0	1
0	A	D
1	B	C

故编码为 A:00 B:01 C:11 D:10

### 编码后的状态表

状态	$X_1=0, X_2=0$	$X_1=0, X_2=1$	$X_1=1, X_2=1$	$X_1=1, X_2=0$	输出
00	00	11	01	00	0
01	01	10	11	00	0
11	11	10	10	01	0
10	10	10	10	10	1

### 状态转移真值表

$x_1 x_2$	00	01	11	10	输出
$y_2 y_1 D_2 D_1$	$y_2 y_1 D_2 D_1$	$y_2 y_1 D_2 D_1$	$y_2 y_1 D_2 D_1$	$y_2 y_1 D_2 D_1$	
00	0 0 0 0	1 1 1 1	0 1 0 1	0 0 0 0	0
01	0 1 0 1	1 0 1 0	1 1 1 1	0 0 0 0	0
11	1 1 1 1	1 0 1 0	1 0 1 0	0 1 0 1	0
10	1 0 1 0	1 0 1 0	1 0 1 0	1 0 1 0	1

$\begin{matrix} x_1x_2 \\ y_2y_1 \end{matrix}$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$$D_2 = \bar{x}_1x_2 + y_2\bar{y}_1 + x_2y_1 + \bar{x}_1y_2$$

$\begin{matrix} x_1x_2 \\ y_2y_1 \end{matrix}$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$$D_1 = x_2\bar{y}_2\bar{y}_1 + x_1x_2\bar{y}_2 + \bar{x}_1\bar{x}_2y_1 + \bar{x}_2y_2y_1$$

由上得激励函数和输出函数表达式如下

$$D_2 = \bar{x}_1x_2 + y_2\bar{y}_1 + x_2y_1 + \bar{x}_1y_2$$

$$D_1 = x_2\bar{y}_2\bar{y}_1 + x_1x_2\bar{y}_2 + \bar{x}_1\bar{x}_2y_1 + \bar{x}_2y_2y_1$$

$$Z = y_2\bar{y}_1$$

由路图如下

